

# ELEC 374 Lab

Phase one

Group 25

Andy Zheng Li: 20124884

William Du: 20100436

## Section 1: VHDL code and Schematics (Datapath and its component)

datapath.vhd

```
1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.std_logic_unsigned.all;
4  use work.components_all.all;
5
6  entity datapath is port (
7  clk: in std_logic;
8  encoderin: in std_logic_vector(31 downto 0);
9  register_enable: in std_logic_vector(31 downto 0);
10 Mdatain: in std_logic_vector(31 downto 0);
11 MDR_Read: in std_logic;
12 ALU_sel: in std_logic_vector(4 downto 0);
13 PC_plus: in std_logic;
14
15 BusMuxOut: out std_logic_vector(31 downto 0);
16 R2out : out std_logic_vector(31 downto 0);
17 R4out : out std_logic_vector(31 downto 0);
18 R5out : out std_logic_vector(31 downto 0);
19 HIout : out std_logic_vector(31 downto 0);
20 LOout : out std_logic_vector(31 downto 0);
21 IRout : out std_logic_vector(31 downto 0);
22 Zout: out std_logic_vector(63 downto 0)
23 );
24 end entity;
25
26 architecture behav of datapath is
27
28 signal in_port, out_port: std_logic_vector(31 downto 0);
29 signal BusMuxIn_R0: std_logic_vector(31 downto 0);
30 signal BusMuxIn_R1: std_logic_vector(31 downto 0);
31 signal BusMuxIn_R2: std_logic_vector(31 downto 0);
32 signal BusMuxIn_R3: std_logic_vector(31 downto 0);
33 signal BusMuxIn_R4: std_logic_vector(31 downto 0);
34 signal BusMuxIn_R5: std_logic_vector(31 downto 0);
35 signal BusMuxIn_R6: std_logic_vector(31 downto 0);
36 signal BusMuxIn_R7: std_logic_vector(31 downto 0);
37 signal BusMuxIn_R8: std_logic_vector(31 downto 0);
38 signal BusMuxIn_R9: std_logic_vector(31 downto 0);
39 signal BusMuxIn_R10: std_logic_vector(31 downto 0);
40 signal BusMuxIn_R11: std_logic_vector(31 downto 0);
41 signal BusMuxIn_R12: std_logic_vector(31 downto 0);
42 signal BusMuxIn_R13: std_logic_vector(31 downto 0);
43 signal BusMuxIn_R14: std_logic_vector(31 downto 0);
44 signal BusMuxIn_R15: std_logic_vector(31 downto 0);
45 signal BusMuxIn_HI: std_logic_vector(31 downto 0);
46 signal BusMuxIn_LO: std_logic_vector(31 downto 0);
47 signal BusMuxIn_Zhigh: std_logic_vector(31 downto 0);
48 signal BusMuxIn_Zlow: std_logic_vector(31 downto 0);
49 signal BusMuxIn_PC: std_logic_vector(31 downto 0);
50 signal BusMuxIn_MDR: std_logic_vector(31 downto 0);
51 signal BusMuxIn_Inport: std_logic_vector(31 downto 0);
52 signal C_sign_extended: std_logic_vector(31 downto 0);
53 signal internalBusMuxOut: std_logic_vector(31 downto 0);
54 signal clr: std_logic;
55 signal default_zeros: std_logic_vector(31 downto 0);
56 signal overflow: std_logic;
57 signal MARout: std_logic_vector(31 downto 0);
58 signal IIRout: std_logic_vector(31 downto 0);
59
60
61 begin
62 default_zeros <= (others => '0');
63 clr<='1';
64 R0 : register32bit port map (internalBusMuxOut, register_enable(0),clr, clk,
65 BusMuxIn_R0);
66 R1 : register32bit port map (internalBusMuxOut, register_enable(1),clr, clk,
67 BusMuxIn_R1);
68 R2 : register32bit port map (internalBusMuxOut, register_enable(2),clr, clk,
69 BusMuxIn_R2);
```

Figure 1: first page of Datapath code

```

67 R3 : register32bit port map (internalBusMuxOut, register_enable(3),clr, clk,
BusMuxIn_R3);
68 R4 : register32bit port map (internalBusMuxOut, register_enable(4),clr, clk,
BusMuxIn_R4);
69 R5 : register32bit port map (internalBusMuxOut, register_enable(5),clr, clk,
BusMuxIn_R5);
70 R6 : register32bit port map (internalBusMuxOut, register_enable(6),clr, clk,
BusMuxIn_R6);
71 R7 : register32bit port map (internalBusMuxOut, register_enable(7),clr, clk,
BusMuxIn_R7);
72 R8 : register32bit port map (internalBusMuxOut, register_enable(8),clr, clk,
BusMuxIn_R8);
73 R9 : register32bit port map (internalBusMuxOut, register_enable(9),clr, clk,
BusMuxIn_R9);
74 R10: register32bit port map (internalBusMuxOut, register_enable(10),clr,
clk,BusMuxIn_R10);
75 R11: register32bit port map (internalBusMuxOut, register_enable(11),clr,
clk,BusMuxIn_R11);
76 R12: register32bit port map (internalBusMuxOut, register_enable(12),clr,
clk,BusMuxIn_R12);
77 R13: register32bit port map (internalBusMuxOut, register_enable(13),clr,
clk,BusMuxIn_R13);
78 R14: register32bit port map (internalBusMuxOut, register_enable(14),clr,
clk,BusMuxIn_R14);
79 R15: register32bit port map (internalBusMuxOut, register_enable(15),clr,
clk,BusMuxIn_R15);
80 HI : register32bit port map (internalBusMuxOut, register_enable(16),clr,
clk,BusMuxIn_HI);
81 LO : register32bit port map (internalBusMuxOut, register_enable(17),clr,
clk,BusMuxIn_LO);
82 PC : register32bit port map (internalBusMuxOut, register_enable(18),clr,
clk,BusMuxIn_PC);
83 IR : register32bit port map (internalBusMuxOut, register_enable(19),clr, clk, IIRout);
84 MD_R: MDR port map (MDR_Read, register_enable(20), clr, clk, internalBusMuxOut, Mdatain,
BusMuxIn_MDR);
85 MAR: register32bit port map (internalBusMuxOut, register_enable(21), clr, clk, MARout);
86 alu datapath : ALU path port map (clk, clr, register_enable(22),
register_enable(23),internalBusMuxOut, internalBusMuxOut, PC_plus, ALU_sel, overflow,
BusMuxIn_Zlow, BusMuxIn_Zhigh);
87 inport_register: register32bit port map ( in_port, register_enable(24),clr,clk,
BusMuxIn_Inport);
88 outport_register: register32bit port map (internalBusMuxOut,register_enable(25), clr,
clk, out_port);
89
90 datapathBus : the_bus port map (BusMuxIn_R0,BusMuxIn_R1, BusMuxIn_R2, BusMuxIn_R3,
91 BusMuxIn_R4, BusMuxIn_R5, BusMuxIn_R6, BusMuxIn_R7, BusMuxIn_R8, BusMuxIn_R9,
BusMuxIn_R10, BusMuxIn_R11,BusMuxIn_R12, BusMuxIn_R13,
92 BusMuxIn_R14, BusMuxIn_R15, BusMuxIn_HI, BusMuxIn_LO, BusMuxIn_Zhigh,BusMuxIn_Zlow,
BusMuxIn_PC, BusMuxIn_MDR, BusMuxIn_Inport,C_sign_extended,
93 default_zeros, default_zeros, default_zeros, default_zeros, default_zeros,
default_zeros, default_zeros, default_zeros, encoderin, internalBusMuxOut);
94
95 BusMuxOut <= internalBusMuxOut;
96 R2out <= BusMuxIn_R2;
97 R4out <= BusMuxIn_R4;
98 R5out <= BusMuxIn_R5;
99 HIout <= BusMuxIn_HI;
100 LOout <= BusMuxIn_LO;
101 Zout(63 downto 32) <= BusMuxIn_Zhigh;
102 Zout(31 downto 0) <= BusMuxIn_Zlow;
103 IIRout <= IIRout;
104 end architecture;

```

Figure 2: second page of Datapath code

## ALU\_path.vhd

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.std_logic_unsigned.all;
4  use ieee.numeric_std.all;
5  use work.components_all.all;
6
7  entity ALU_path is port(
8  clk:in std_logic;
9  clr:in std_logic;
10 Y_enable:in std_logic;
11 Z_enable: in std_logic;
12 In1: in std_logic_vector(31 downto 0);
13 In2: in std_logic_vector(31 downto 0);
14 PC_plus: in std_logic;
15 ALU_sel: in std_logic_vector(4 downto 0);
16 overflow: out std_logic;
17 ToLow:out std_logic_vector(31 downto 0);
18 ToHi: out std_logic_vector(31 downto 0)
19 );
20 end entity ALU_path;
21
22 architecture structure of ALU_path is
23 signal Yout: std_logic_vector(31 downto 0);
24 signal Zin: std_logic_vector(63 downto 0);
25 signal ALU_out: std_logic_vector(63 downto 0);
26 signal PCinc: std_logic_vector(63 downto 0);
27
28 begin
29 register_Y: register32bit port map (In1, Y_enable, clr, clk, Yout);
30 the_alu: alu port map (Yout, In2, ALU_sel, overflow, ALU_out);
31 register_Z: register64bit port map (Zin, Z_enable, clr, clk, ToLow, ToHi);
32
33 PCinc(31 downto 0) <= std_logic_vector(unsigned(In1)+1); --increment the content of PC
    by 1
34 PCinc(63 downto 32) <= (others=>'0');
35 Zin <= PCinc when PC_plus = '1' else
36     ALU_out; -- the mux between alu and Z
37
38 end architecture structure;

```

Figure 3: ALU path code

## register32bit.vhd

```

1  Library ieee;
2  Use ieee.std_logic_1164.ALL;
3  Use ieee.std_logic_arith.ALL;
4  Use ieee.std_logic_unsigned.ALL;
5
6  entity register32bit is Port(
7  D : in std_logic_vector (31 downto 0);
8  ld : in std_logic;
9  clr : in std_logic;
10 clk : in std_logic;
11 Q: out std_logic_vector (31 downto 0));
12
13 end entity register32bit;
14
15
16 architecture behav of register32bit is
17 begin
18     process(clk, clr)
19     begin
20         if clr = '0' then
21             Q <= (others=>'0');
22         elsif (clk'event and clk='1') then
23             if ld = '1' then
24                 Q <= D;
25             end if;
26         end if;
27     end process;
28 end behav;

```

Figure 4: 32bit register code

register64bit.vhd

```
1  Library ieee;
2  Use ieee.std_logic_1164.ALL;
3  Use ieee.std_logic_arith.ALL;
4  Use ieee.std_logic_unsigned.ALL;
5
6  entity register64bit is Port(
7  D : in std_logic_vector (63 downto 0);
8  ld : in std_logic;
9  clr : in std_logic;
10 clk : in std_logic;
11 Q0: out std_logic_vector (31 downto 0);
12 Q1: out std_logic_vector (31 downto 0)
13 );
14
15 end entity register64bit; --for register Z
16
17
18 architecture behav of register64bit is
19 begin
20     process(clk, clr)
21     begin
22         if clr = '0' then --active low
23             Q0<= (others=>'0');
24             Q1<= (others=>'0');
25         elsif (clk'event and clk='1') then
26             if ld = '1' then
27                 Q0 <= D(31 downto 0);
28                 Q1 <= D(63 downto 32);
29             end if;
30         end if;
31     end process;
32 end behav;
```

Figure 5: 64bit register code



# alu.vhd

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.std_logic_unsigned.all;
4  --use ieee.numeric_std.all;
5  use work.components_all.all;
6
7  entity alu is port(
8  A : in std_logic_vector(31 downto 0);
9  B : in std_logic_vector(31 downto 0);
10 ALU_sel : in std_logic_vector(4 downto 0);
11 overflow : out std_logic;
12 C : out std_logic_vector(63 downto 0)
13 );
14 end entity alu;
15
16 architecture behav of alu is
17 signal Mulout: std_logic_vector(63 downto 0);
18 signal Divout: std_logic_vector(63 downto 0);
19 signal addorsub: std_logic;
20 signal addsuboverflow: std_logic;
21 signal addsubout: std_logic_vector(31 downto 0);
22 signal rorout:std_logic_vector(31 downto 0);
23 signal rolout:std_logic_vector(31 downto 0);
24 signal shrout: std_logic_vector(31 downto 0);
25 signal shlout: std_logic_vector(31 downto 0);
26 signal negout: std_logic_vector(31 downto 0);
27
28 begin
29 aluMul: booth logic port map (A, B, Mulout);
30 aluDiv: lpm_divide port map(B, A, Divout(31 downto 0), Divout(63 downto 32));
31 aluAddSub: lpm_add_sua port map (addorsub, A, B, addsuboverflow, addsubout);
32 aluRor: ror32 port map (A, B(4 downto 0), rorout);
33 aluRol: rol32 port map (A, B(4 downto 0), rolout);
34 aluShl: shl32 port map (A, B, shlout);
35 aluShr: shr32 port map (A, B, shrout);
36 aluNeg: negate32 port map(B, negout);
37
38 process(A,B,ALU_sel,Mulout,Divout,addorsub,addsuboverflow,addsubout,negout, shlout,
39 shrout, rorout, rolout) is
40 begin
41 addorsub <= '0';
42 overflow <= '0';
43
44 if (ALU_sel = "01001") then
45 C(31 downto 0) <= A and B;
46 C(63 downto 32) <= (others => '0');
47
48 elsif (ALU_sel = "01010") then
49 C(31 downto 0) <= A or B;
50 C(63 downto 32) <= (others => '0');
51
52 elsif (ALU_sel = "01011") then
53 C(31 downto 0) <= A or B;
54 C(63 downto 32) <= (others => '0');
55
56 elsif (ALU_sel = "10001") then
57 C(31 downto 0) <= not B;
58 C(63 downto 32) <= (others => '0');
59
60 elsif (ALU_sel = "10000") then
61 C(31 downto 0) <= negout;
62 C(63 downto 32) <= (others => '0');
63
64 elsif (ALU_sel = "00101") then
65 C(31 downto 0) <= shrout;
66 C(63 downto 32) <= (others => '0');
67
68 elsif (ALU_sel = "00110") then

```

Figure 6: first page of ALU code

```

69      C(31 downto 0) <= shlout;
70      C(63 downto 32) <= (others => '0');
71
72      elsif (ALU_sel = "00111") then
73          C(31 downto 0) <= rorout;
74          C(63 downto 32) <= (others => '0');
75
76      elsif (ALU_sel = "01000") then
77          C(31 downto 0) <= rolout;
78          C(63 downto 32) <= (others => '0');
79
80      elsif (ALU_sel = "01110") then
81          C <= Mulout;
82
83      elsif (ALU_sel = "01111") then
84          C <= Divout;
85
86      elsif (ALU_sel = "00011") then
87          addorsub <= '1';
88          C(31 downto 0) <= addsubout;
89          C(63 downto 32) <= (others => '0');
90          overflow <= addsuboverflow;
91
92      elsif (ALU_sel = "00100") then
93          addorsub <= '0';
94          C(31 downto 0) <= addsubout;
95          C(63 downto 32) <= (others => '0');
96          overflow <= addsuboverflow;
97      else
98          C <= (others => '0');
99
100  end if ;
101 end process;
102 end architecture behav;

```

Figure 7: second page of ALU code

lpm\_add\_sub (built-in function)

 


Figure 8: schematic of built-in add/subtract function

lpm\_divide (built-in function)

 


Figure 9: schematic of built-in divide function

## booth\_logic.vhd

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.std_logic_unsigned.all;
4  use ieee.numeric_std.all;
5
6  entity booth_logic is port(
7    Mucand : in std_logic_vector(31 downto 0);
8    MUser : in std_logic_vector(31 downto 0);
9    product : out std_logic_vector(63 downto 0)
10 );
11 end entity booth_logic;
12
13 architecture logic of booth_logic is
14 begin
15   process(Mucand, MUser)
16     variable sum : signed(63 downto 0) := (others => '0');
17     variable M : signed(63 downto 0);
18     variable q : signed(32 downto 0);
19   begin
20     M := resize(signed(Mucand), M'length);
21     q(0) := '0';
22     q(32 downto 1) := signed(MUser);
23     for i in 0 to 31 loop
24       if(q(0) = '0' and q(1) = '1') then
25         sum := sum - (M sll i);
26       elsif(q(0) = '1' and q(1) = '0') then
27         sum := sum + (M sll i);
28       end if;
29       q := q srl 1;
30     end loop;
31     product <= std_logic_vector(sum);
32     sum := (others => '0');
33   end process;
34 end architecture logic;

```

Figure 10: booth multiplication code

## negate32.vhd

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.std_logic_unsigned.all;
4  use ieee.numeric_std.all;
5
6  entity negate32 is
7    port(
8      input: in std_logic_vector(31 downto 0);
9      output : out std_logic_vector(31 downto 0)
10 );
11 end entity negate32;
12
13 architecture logic of negate32 is
14 begin
15   output <= std_logic_vector(signed(not input) + 1);
16 end architecture logic;

```

Figure 11: two's compliment code



rol32.vhd

```
1  LIBRARY ieee;
2  USE ieee.std_logic_1164.all;
3
4  LIBRARY lpm;
5  USE lpm.all;
6
7  ENTITY rol32 IS
8      PORT
9      (
10         data      : IN STD_LOGIC_VECTOR (31 DOWNTO 0);
11         distance   : IN STD_LOGIC_VECTOR (4 DOWNTO 0);
12         result     : OUT STD_LOGIC_VECTOR (31 DOWNTO 0)
13     );
14 END rol32;
15
16
17 ARCHITECTURE SYN OF rol32 IS
18
19     SIGNAL sub_wire0 : STD_LOGIC_VECTOR (31 DOWNTO 0);
20     SIGNAL sub_wire1 : STD_LOGIC ;
21
22
23
24     COMPONENT lpm_clshift
25     GENERIC (
26         lpm_shifttype : STRING;
27         lpm_type       : STRING;
28         lpm_width      : NATURAL;
29         lpm_widthdist  : NATURAL
30     );
31     PORT (
32         data      : IN STD_LOGIC_VECTOR (31 DOWNTO 0);
33         direction : IN STD_LOGIC ;
34         distance   : IN STD_LOGIC_VECTOR (4 DOWNTO 0);
35         result     : OUT STD_LOGIC_VECTOR (31 DOWNTO 0)
36     );
37     END COMPONENT;
38
39 BEGIN
40     sub_wire1 <= '0';
41     result <= sub_wire0(31 DOWNTO 0);
42
43     LPM_CLSHIFT_component : LPM_CLSHIFT
44     GENERIC MAP (
45         lpm_shifttype => "ROTATE",
46         lpm_type => "LPM_CLSHIFT",
47         lpm_width => 32,
48         lpm_widthdist => 5
49     )
50     PORT MAP (
51         data => data,
52         direction => sub_wire1,
53         distance => distance,
54         result => sub_wire0
55     );
56
57
58
59 END SYN;
```

Figure 12: rotate left code

ror32.vhd

```
1  LIBRARY ieee;
2  USE ieee.std_logic_1164.all;
3
4  LIBRARY lpm;
5  USE lpm.all;
6
7  ENTITY ror32 IS
8  PORT
9  (
10     data      : IN STD_LOGIC_VECTOR (31 DOWNTO 0);
11     distance   : IN STD_LOGIC_VECTOR (4 DOWNTO 0);
12     result     : OUT STD_LOGIC_VECTOR (31 DOWNTO 0)
13 );
14 END ror32;
15
16
17 ARCHITECTURE SYN OF ror32 IS
18
19     SIGNAL sub_wire0 : STD_LOGIC_VECTOR (31 DOWNTO 0);
20     SIGNAL sub_wire1 : STD_LOGIC ;
21
22
23
24     COMPONENT lpm_clshift
25     GENERIC (
26         lpm_shifttype : STRING;
27         lpm_type       : STRING;
28         lpm_width      : NATURAL;
29         lpm_widthdist  : NATURAL
30     );
31     PORT (
32         data      : IN STD_LOGIC_VECTOR (31 DOWNTO 0);
33         direction  : IN STD_LOGIC ;
34         distance   : IN STD_LOGIC_VECTOR (4 DOWNTO 0);
35         result     : OUT STD_LOGIC_VECTOR (31 DOWNTO 0)
36     );
37 END COMPONENT;
38
39 BEGIN
40     sub_wire1 <= '1';
41     result    <= sub_wire0(31 DOWNTO 0);
42
43     LPM_CLSHIFT_component : LPM_CLSHIFT
44     GENERIC MAP (
45         lpm_shifttype => "ROTATE",
46         lpm_type       => "LPM_CLSHIFT",
47         lpm_width      => 32,
48         lpm_widthdist  => 5
49     )
50     PORT MAP (
51         data      => data,
52         direction => sub_wire1,
53         distance  => distance,
54         result    => sub_wire0
55     );
56
57
58
59 END SYN;
```

Figure 13: rotate right code

### shl32.vhd

```
1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.std_logic_unsigned.all;
4  use ieee.numeric_std.all;
5
6  entity shl32 is port(
7      input0 : in std_logic_vector(31 downto 0);
8      input1 : in std_logic_vector(31 downto 0);
9      output  : out std_logic_vector(31 downto 0)
10 );
11 end entity shl32;
12
13 architecture logic of shl32 is
14 begin
15     output <= std_logic_vector(shift_left(unsigned(input0), to_integer(signed(input1))));
16 end architecture logic;
```

Figure 14: shift left code

### shr32.vhd

```
1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.std_logic_unsigned.all;
4  use ieee.numeric_std.all;
5
6  entity shr32 is port(
7      input0 : in std_logic_vector(31 downto 0);
8      input1 : in std_logic_vector(31 downto 0);
9      output  : out std_logic_vector(31 downto 0)
10 );
11 end entity shr32;
12
13 architecture logic of shr32 is
14 begin
15     output <= std_logic_vector(shift_right(unsigned(input0), to_integer(signed(input1))));
16 end architecture logic;
```

Figure 15: shift right code

the\_bus.vhd

```
1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.std_logic_unsigned.all;
4  use work.components_all.all;
5
6  entity the_bus is port (
7      muxIn0      : in std_logic_vector (31 downto 0);
8      muxIn1      : in std_logic_vector (31 downto 0);
9      muxIn2      : in std_logic_vector (31 downto 0);
10     muxIn3      : in std_logic_vector (31 downto 0);
11     muxIn4      : in std_logic_vector (31 downto 0);
12     muxIn5      : in std_logic_vector (31 downto 0);
13     muxIn6      : in std_logic_vector (31 downto 0);
14     muxIn7      : in std_logic_vector (31 downto 0);
15     muxIn8      : in std_logic_vector (31 downto 0);
16     muxIn9      : in std_logic_vector (31 downto 0);
17     muxIn10     : in std_logic_vector (31 downto 0);
18     muxIn11     : in std_logic_vector (31 downto 0);
19     muxIn12     : in std_logic_vector (31 downto 0);
20     muxIn13     : in std_logic_vector (31 downto 0);
21     muxIn14     : in std_logic_vector (31 downto 0);
22     muxIn15     : in std_logic_vector (31 downto 0);
23     muxIn16     : in std_logic_vector (31 downto 0);
24     muxIn17     : in std_logic_vector (31 downto 0);
25     muxIn18     : in std_logic_vector (31 downto 0);
26     muxIn19     : in std_logic_vector (31 downto 0);
27     muxIn20     : in std_logic_vector (31 downto 0);
28     muxIn21     : in std_logic_vector (31 downto 0);
29     muxIn22     : in std_logic_vector (31 downto 0);
30     muxIn23     : in std_logic_vector (31 downto 0);
31     muxIn24     : in std_logic_vector (31 downto 0);
32     muxIn25     : in std_logic_vector (31 downto 0);
33     muxIn26     : in std_logic_vector (31 downto 0);
34     muxIn27     : in std_logic_vector (31 downto 0);
35     muxIn28     : in std_logic_vector (31 downto 0);
36     muxIn29     : in std_logic_vector (31 downto 0);
37     muxIn30     : in std_logic_vector (31 downto 0);
38     muxIn31     : in std_logic_vector (31 downto 0);
39     encoder32In : in std_logic_vector(31 downto 0);
40     BusMuxOut   : out std_logic_vector(31 downto 0)
41 );
42 end entity the_bus;
43
44 architecture structure of the_bus is
45     signal Mux_sel: std_logic_vector(4 downto 0);
46
47     begin
48     Bus_encoder: encoder32to5 port map(encoder32In, Mux_sel);
49     Bus_Mux: lpm_mua port map (muxIn0, muxIn1, muxIn2, muxIn3, muxIn4, muxIn5,
50     muxIn6, muxIn7, muxIn8, muxIn9, muxIn10, muxIn11, muxIn12, muxIn13,
51     muxIn14, muxIn15, muxIn16, muxIn17, muxIn18, muxIn19, muxIn20, muxIn21,
52     muxIn22, muxIn23, muxIn24, muxIn25, muxIn26, muxIn27, muxIn28, muxIn29,
53     muxIn30, muxIn31, Mux_sel, BusMuxOut);
54
55 end architecture structure;
```

Figure 16: bus code

## encoder32to5.vhd

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.std_logic_unsigned.all;
4
5  entity encoder32to5 is port(
6      input : in std_logic_vector(31 downto 0);
7      output: out std_logic_vector(4 downto 0)
8  );
9  end entity encoder32to5;
10
11 architecture behav of encoder32to5 is
12 begin
13     output <= "00000" when (input = "00000000000000000000000000000001")
14         else "00001" when (input = "00000000000000000000000000000010")
15         else "00010" when (input = "000000000000000000000000000000100")
16         else "00011" when (input = "0000000000000000000000000000001000")
17         else "00100" when (input = "00000000000000000000000000000010000")
18         else "00101" when (input = "000000000000000000000000000000100000")
19         else "00110" when (input = "0000000000000000000000000000001000000")
20         else "00111" when (input = "00000000000000000000000000000010000000")
21         else "01000" when (input = "0000000000000000000000000000100000000")
22         else "01001" when (input = "00000000000000000000000000001000000000")
23         else "01010" when (input = "000000000000000000000000000010000000000")
24         else "01011" when (input = "0000000000000000000000000000100000000000")
25         else "01100" when (input = "0000000000000000000000000000100000000000")
26         else "01101" when (input = "0000000000000000000000000000100000000000")
27         else "01110" when (input = "0000000000000000000000000000100000000000")
28         else "01111" when (input = "0000000000000000000000000000100000000000")
29         else "10000" when (input = "0000000000000000000000000000100000000000")
30         else "10001" when (input = "0000000000000000000000000000100000000000")
31         else "10010" when (input = "0000000000000000000000000000100000000000")
32         else "10011" when (input = "0000000000000000000000000000100000000000")
33         else "10100" when (input = "0000000000000000000000000000100000000000")
34         else "10101" when (input = "0000000000000000000000000000100000000000")
35         else "10110" when (input = "0000000000000000000000000000100000000000")
36         else "10111" when (input = "0000000000000000000000000000100000000000")
37         else "11000" when (input = "0000000000000000000000000000100000000000")
38         else "11001" when (input = "0000000000000000000000000000100000000000")
39         else "11010" when (input = "0000000000000000000000000000100000000000")
40         else "11011" when (input = "0000000000000000000000000000100000000000")
41         else "11100" when (input = "0000000000000000000000000000100000000000")
42         else "11101" when (input = "0000000000000000000000000000100000000000")
43         else "11110" when (input = "0000000000000000000000000000100000000000")
44         else "11111";
45 end architecture behav;

```

Figure 17: 32-to-5 encoder

## lpm\_mua (built-in function)

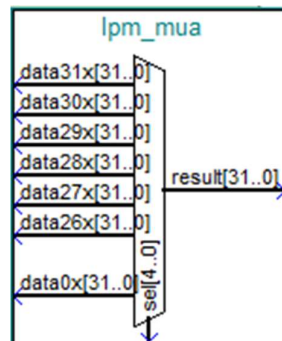


Figure 18: schematic of built-in MUA function



## MDR.vhd

```
1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.std_logic_unsigned.all;
4  use work.components_all.all;
5
6  entity MDR is port(
7    MDMux_read: in std_logic;
8    MDR_enable: in std_logic;
9    clr: in std_logic;
10   clk: in std_logic;
11   MDR_in1: in std_logic_vector(31 downto 0);
12   MDR_in2: in std_logic_vector(31 downto 0); --1 is from bus, 2 is from memory
13   MDR_out: out std_logic_vector(31 downto 0)
14 );
15 end entity MDR;
16
17 architecture behav of MDR is
18   signal MDMux_out: std_logic_vector(31 downto 0);
19   begin
20     MDMux_out <= MDR_in1 when MDMux_read = '0' else
21                 MDR_in2;
22   The_MDR: register32bit port map(MDMux_out, MDR_enable, clr, clk, MDR_out);
23
24 end architecture behav;
```

Figure 19: MDR code

## Section 2: Testbench

Testbench file for “and” instruction:

```
1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity datapath_and_tb is
5  end;
6
7  architecture logic of datapath_and_tb is
8
9  signal clk_tb : std_logic;
10 signal clr_tb : std_logic;
11 signal IncPC_tb : std_logic;
12 signal MDRRead_tb : std_logic;
13 signal aluOp : std_logic_vector(4 downto 0);
14 signal encoderIn_tb : std_logic_vector(31 downto 0);
15 signal RegEnable_tb : std_logic_vector(31 downto 0);
16 signal Mdatain_tb : std_logic_vector(31 downto 0);
17
18 signal BusMuxOut_tb, IRout_tb: std_logic_vector(31 downto 0);
19 signal Zout_tb: std_logic_vector(63 downto 0);
20 signal R2out_tb: std_logic_vector(31 downto 0);
21 signal R4out_tb: std_logic_vector(31 downto 0);
22 signal R5out_tb: std_logic_vector(31 downto 0);
23 signal HIout_tb, LOout_tb: std_logic_vector(31 downto 0);
24 type state is (default, Reg_load1a, Reg_load1b, Reg_load2a, Reg_load2b, Reg_load3a,
25 Reg_load3b, T0, T1, T2, T3, T4, T5, T6);
26 signal present_state: State := default;
27
28 component datapath
29 port (
30     clk: in std_logic;
31     encoderin: in std_logic_vector(31 downto 0);
32     register_enable : in std_logic_vector(31 downto 0);
33     Mdatain : in std_logic_vector(31 downto 0);
34     MDR_Read : in std_logic;
35     ALU_sel : in std_logic_vector(4 downto 0);
36     PC_plus : in std_logic;
37
38     BusMuxOut: out std_logic_vector(31 downto 0);
39     R2out : out std_logic_vector(31 downto 0);
40     R4out : out std_logic_vector(31 downto 0);
41     R5out : out std_logic_vector(31 downto 0);
42     HIout : out std_logic_vector(31 downto 0);
43     LOout : out std_logic_vector(31 downto 0);
44     IRout : out std_logic_vector(31 downto 0);
45     Zout : out std_logic_vector(63 downto 0)
46 );
47 end component;
48
49 begin
50 Test : datapath port map (clk_tb, encoderIn_tb, RegEnable_tb, Mdatain_tb, MDRRead_tb,
51 aluOp, IncPC_tb, BusMuxOut_tb,
52 R2out_tb, R4out_tb, R5out_tb, HIout_tb, LOout_tb, IRout_tb, Zout_tb);
53
54 clk_process: process
55 begin
56     clk_tb <= '1', '0' after 10 ns;
57     wait for 20 ns;
58 end process clk_process;
59
60 process(clk_tb)
61 begin
62     if(clk_tb'event and clk_tb = '1') then
63         case present_state is
64             when default =>
65                 present_state <= Reg_load1a;
66             when Reg_load1a =>
67                 present_state <= Reg_load1b;
68             when Reg_load1b =>
69                 present_state <= Reg_load2a;
70             when Reg_load2a =>
```

Figure 20: first page of testbench code for “and” instruction

```

68         when Reg_load2a =>
69             present_state <= Reg_load2b;
70         when Reg_load2b =>
71             present_state <= Reg_load3a;
72         when Reg_load3a =>
73             present_state <= Reg_load3b;
74         when Reg_load3b =>
75             present_state <= T0;
76         when T0 =>
77             present_state <= T1;
78         when T1 =>
79             present_state <= T2;
80         when T2 =>
81             present_state <= T3;
82         when T3 =>
83             present_state <= T4;
84         when T4 =>
85             present_state <= T5;
86         when T5 =>
87             present_state <= T6;
88         when others =>
89             end case;
90     end if;
91 end process;
92
93 process (present_state)
94 begin
95     case present_state is
96     when default =>
97         IncPC_tb <= '0';
98         MDRRead_tb <= '0';
99         aluOp <= (others => '0');
100        Mdatain_tb <= (others => '0');
101        encoderIn_tb <= (others => '0');
102        RegEnable_tb <= (others => '0');
103    when Reg_load1a =>
104        Mdatain_tb <= x"000000022";
105        MDRRead_tb <= '0', '1' after 10 ns, '0' after 25 ns;
106        RegEnable_tb <= (others=>'0'), (20=>'1', others=>'0') after 10 ns,
107        (others=>'0') after 25 ns; -- MDRin enable (the 20th bit of regenable);
108    when Reg_load1b =>
109        encoderIn_tb <= (others=>'0'), (21 => '1', others => '0') after 10 ns,
110        (others=>'0') after 25 ns;
111        RegEnable_tb <= (others=>'0'), (2 => '1', others => '0') after 10 ns,
112        (others=>'0') after 25 ns;
113    when Reg_load2a =>
114        Mdatain_tb <= x"000000024";
115        MDRRead_tb <= '0', '1' after 10 ns, '0' after 25 ns;
116        RegEnable_tb <= (others=>'0'), (20=>'1', others=>'0') after 10 ns,
117        (others=>'0') after 25 ns; -- MDRin
118    when Reg_load2b =>
119        encoderIn_tb <= (others=>'0'), (21 => '1', others => '0')after 10 ns,
120        (others=>'0') after 25 ns;
121        RegEnable_tb <= (others=>'0'), (4 => '1', others => '0')after 10 ns,
122        (others=>'0') after 25 ns; -- R4 load_en
123    when Reg_load3a =>
124        Mdatain_tb <= x"000000026";
125        MDRRead_tb <= '0', '1' after 10 ns, '0' after 25 ns;
126        RegEnable_tb <= (others=>'0'), (20=>'1', others=>'0') after 10 ns,
127        (others=>'0') after 25 ns;
128    when Reg_load3b =>
129        encoderIn_tb <= (others=>'0'), (21 => '1', others => '0')after 10 ns,
130        (others=>'0') after 25 ns;
131        RegEnable_tb <= (others=>'0'), (5 => '1', others => '0')after 10 ns,

```

Figure 21: second page of testbench code for “and” instruction

```

129      (others=>'0') after 25 ns; -- R5 load_en
130
131  when T0 =>
132      encoderIn_tb <= (20 => '1', others => '0'); -- pc encoder
133      RegEnable_tb <= (21 => '1', 23 => '1', others => '0'); -- MAR, Zin
134      IncPC_tb <= '1';
135
136  when T1 =>
137      encoderIn_tb <= (19 => '1', others => '0'); -- zlow encoder
138      RegEnable_tb <= (18 => '1', 20 => '1', others => '0'); -- pc load_en, MDR
139      load_en
140      IncPC_tb <= '0';
141      MDRRead_tb <= '1';
142      Mdatain_tb <= x"4A920000"; -- opcode for "and R5, R2, R4"
143
144  when T2 =>
145      MDRRead_tb <= '0';
146      Mdatain_tb <= (others => '0');
147      encoderIn_tb <= (21 => '1', others => '0'); -- MDR encoder input
148      RegEnable_tb <= (19 => '1', others => '0'); -- IR load_en
149
150  when T3 =>
151      encoderIn_tb <= (2 => '1', others => '0'); -- R2 encoder input
152      RegEnable_tb <= (22 => '1', others => '0'); -- RY load_en
153
154  when T4 =>
155      encoderIn_tb <= (4 => '1', others => '0'); -- R4 encoder input
156      aluOp <= "01001";
157      RegEnable_tb <= (23 => '1', others => '0'); -- RZ load_en
158
159  when T5 =>
160      encoderIn_tb <= (19 => '1', others => '0'); -- Zlow encoder
161      RegEnable_tb <= (5 => '1', 17 => '1', others => '0'); -- R5, LO load_en
162
163  when T6 =>
164      encoderIn_tb <= (18 => '1', others => '0'); -- Zhigh encoder
165      RegEnable_tb <= (16 => '1', others => '0'); -- HI load_en
166  when others =>
167      end case;
168  end process;
169  end architecture;

```

Figure 22: third page of testbench code for “and” instruction

The above printout of the VHDL code for the “and” instruction testbench is similar to most other testbenches other than the “negative” and “not” instruction testbenches. The ones that are similar to the “and” instruction testbench differ in only three places. The value of the instruction opcode and the value of the ALU opcode. The value in registers is occasionally different in order to properly show the correct functionality of the instruction. The “negative” and “not” instruction test benches are similar to each other and, on top of the differences mentioned previously, differ from the other testbenches by having one less state due to needing less registers.

## Section 3: Functional Simulation and Demonstration

The screenshots of the testbench files for all the functional simulation result shown below have been provided in Section 2: Testbench above.

### 3.a and R5, R2, R4

 


Figure 23: Functional simulation for AND operation

- (1) R2 is initialized with value 34 in decimal (or hex "0000\_0022" / "100010" in binary)
- (2) R4 is initialized with value 36 in decimal (or hex "0000\_0024" / "100100" in binary)
- (3) R5 is initialized with value 38 in decimal (or hex "0000\_0026" / "100110" in binary)

**T0:** PCout signal is for encoder to select PC as input to the bus, incPC turns to '1' (to increment the PC), MARin and Zin enables the registers MAR and Z, respectively.

**T1:** Zlowout signal for encoder selects the lower half of register as input to the bus, PCin enables the PC, MDRin enables the MDR to accept data, read signal select Mdata as input to the MDR, the Mdatain is loaded with the instruction x"4A920000" for the AND operation.

**T2:** MDRout signal causes the bus to select the output of MDR as input, IRin enables the IR.

**T3:** R2out is the input to the bus encoder for selection of R2 as the input to the bus, Yin enables the Y register.

**T4:** R4out is the input to the bus encoder for selection of R4 as the input to the bus, AND is the opcode signal for the ALU to performance AND operation, Zin enables register Z to accept data.

**T5:** Zlowout signal ensure the bus takes the lower 32-bit of the Z register (the result of the AND operation) as the input, R5in enables R5 to accept data coming from the bus.

- (4) As we can see in Figure 23 above, in the end of state T6 (State T6 is an extra step for the upper 32-bit of register Z), the result of the AND operation is equal to 100000 which makes logical sense (100010 and 100100 = 100000). The IRout also matches the instruction opcode for this operation, which is x"4A920000". The ALU signal is 01001 which is the opcode for the AND operation.



3.b or R5, R2, R4

 


Figure 24:Functional simulation for OR operation

- (1) R2 is initialized with value 34 in decimal (or hex "0000\_0022"/ "100010" in binary)
- (2) R4 is initialized with value 36 in decimal (or hex "0000\_0024"/ "100100" in binary)
- (3) R5 is initialized with value 38 in decimal (or hex "0000\_0026"/ "100110" in binary)

The control sequences are mostly the same as the AND operation in 3.a and R5, R2, R4, except the OR operation has a different instruction and ALU opcode which is equal to **x"52920000"** and **01010**, respectively.

- (4) As we can see in Figure 24 above, in the end of state T6 (State T6 is an extra step for the upper 32-bit of register Z), the result of the OR operation is equal to 100110 which makes logical sense ( $100010$  or  $100100 = 100110$ ).

3.c add R5, R2, R4

 


Figure 25: Functional Simulation for ADD operation

- (1) R2 is initialized with value 34 in decimal (or hex "0000\_0022"/ "100010" in binary)
- (2) R4 is initialized with value 36 in decimal (or hex "0000\_0024"/ "100100" in binary)
- (3) R5 is initialized with value 38 in decimal (or hex "0000\_0026"/ "100110" in binary)

The control sequences are mostly the same as the AND operation in 3.a and R5, R2, R4, except the ADD operation has a different instruction and ALU opcode which is equal to **x"1A920000"** and **00011**, respectively.

- (4) As we can see in Figure 25 above, in the end of state T6 (State T6 is an extra step for the upper 32-bit of register Z), the result of the ADD operation is equal to 1000110 (34+36 = 70 (in decimal)) which makes logical sense.

3.d sub R5, R2, R4

 


Figure 26: Functional Simulation of sub operation

- (1) R4 is initialized with value 34 in decimal (or hex "0000\_0022"/ "100010" in binary)
- (2) R2 is initialized with value 36 in decimal (or hex "0000\_0024"/ "100100" in binary)
- (3) R5 is initialized with value 38 in decimal (or hex "0000\_0026"/ "100110" in binary)

The control sequences are mostly the same as the ADD operation in 3.c `add R5, R2, R4`, except the subtraction operation has a different instruction and ALU opcode which is equal to **x"22920000"** and **00100**, respectively.

- (4) As we can see in Figure 26 above, in the end of state T6 (State T6 is an extra step for the upper 32-bit of register Z), the result (which is inside both R5 and the LO register) of the sub operation is equal to 00010 ( $36 - 34 = 2$  (in decimal)) which makes logical sense.

### 3.e mul R2, R4

 


Figure 27:Functional Simulation of mul operation

- (1) R2 is initialized with value 8 in decimal (or hex "0000\_0008"/ "1000" in binary)
- (2) R4 is initialized with value 4 in decimal (or hex "0000\_0004"/ "0010" in binary)

The control sequences are mostly the same as the ADD operation in 3.c add R5, R2, R4, except the MUL operation has a different instruction and ALU opcode which is equal to **x"72920000"** and **01110**, respectively. In addition, the higher 32-bit of register Z is outputted to the HI register at state T6.

- (4) As we can see in Figure 27 above, in the end of state T6, the result of the MUL operation is equal to 100000 (8 \* 4 = 32 (in decimal)) which makes logical sense. The result of the operation is stored in the LO register as expected. The R5out in the above diagram is included only for convenience (not making change to the testbench code), the actual operation does not involve R5.

3.f div R2, R4

 


Figure 28: Functional Simulation for div operation

- (1) R2 is initialized with value 9 in decimal (or hex "0000\_0009" / "1001" in binary)
- (2) R4 is initialized with value 4 in decimal (or hex "0000\_0004" / "0010" in binary)

The control sequences are mostly the same as the MUL operation in 3.e mul R2, R4, except the div operation has a different instruction and ALU opcode which is equal to **x"7A920000"** and **01111**, respectively. In addition, the higher 32-bit of register Z is outputted to the HI register at state T6.

(4) As we can see in Figure 28 above, in the end of state T6, the result of the div operation is equal to 2R1 (9/4=2R1(in decimal)) which makes logical sense. The quotient (10 = 2 (in decimal)) of the operation is stored in the LO register, and the remainder (01 = 1(in decimal)) is stored in the HI register as expected. The R5out in the above diagram is included only for convenience (not making change to the testbench code), the actual operation does not involve R5.



### 3.g shr R5, R2, R4

 


Figure 29:Functional Simulation of shr operation

- (1) R2 is initialized with value 34 in decimal (or hex "0000\_0022" / "100010" in binary)
- (2) R4 is initialized with value 2 in decimal (or hex "0000\_0002" / "000010" in binary)
- (3) R5 is initialized with value 38 in decimal (or hex "0000\_0026" / "100110" in binary)

The control sequences are mostly the same as the SUB operation in 3.d sub R5, R2, R4, except the SHR operation has a different instruction and ALU opcode which is equal to **x"2A920000"** and **00101**, respectively.

- (4) As we can see in Figure 29 above, in the end of state T6, the result of the SHR operation is equal to 1000 which makes logical sense. The content in R2 (100010) is shifted to the right by 2 bits (content in R4), which results in 10000 and it is stored in R5. The initial value stored in R5 is overwritten.

### 3.h shl R5, R2, R4

 


Figure 30:Functional Simulation of shl operation

- (1) R2 is initialized with value 34 in decimal (or hex "0000\_0022" / "100010" in binary)
- (2) R4 is initialized with value 2 in decimal (or hex "0000\_0002" / "000010" in binary)
- (3) R5 is initialized with value 38 in decimal (or hex "0000\_0026" / "100110" in binary)

The control sequences are mostly the same as the SHR operation in 3.g shr R5, R2, R4, except the SHL operation has a different instruction and ALU opcode which is equal to **x"32920000"** and **00110**, respectively.

- (4) As we can see in Figure 30 above, in the end of state T6, the result of the SHL operation is equal to 10001000 which makes logical sense. The content in R2 (100010) is shifted to the left by 2 bits (content in R4), which results in 10001000 and it is stored in R5. The initial value stored in R5 is overwritten.

### 3.i ror R5, R2, R4

 


Figure 31:Functional Simulation of ror operation

- (1) R2 is initialized with value 34 in decimal (or hex "0000\_0022" / "100010" in binary)
- (2) R4 is initialized with value 4 in decimal (or hex "0000\_0004" / "000010" in binary)
- (3) R5 is initialized with value 38 in decimal (or hex "0000\_0026" / "100110" in binary)

The control sequences are mostly the same as the SHR operation in 3.g shr R5, R2, R4, except the ROR operation has a different instruction and ALU opcode which is equal to x"3A920000" and 00111, respectively.

- (4) As we can see in Figure 31 above, in the end of state T6, the result of the ROR operation is equal to 001000000000000000000000000010 which makes logical sense. The content in R2 (100010) is rotated to the right by 4 bits (content in R4), which means the four most significant bits (0010) will become the four least significant bit of the 32-bit number since it got rotated to the right.

[illegible]

- (1) R2 is initialized with value 34 in decimal (or hex "0000\_0022"/ "100010" in binary)
- (2) R4 is initialized with value 4 in decimal (or hex "0000\_0004"/ "000010" in binary)
- (3) R5 is initialized with value 38 in decimal (or hex "0000\_0026"/ "100110" in binary)

(4) As we can see in Figure 32 above, in the end of state T6, the result of the ROL operation is equal to **1000100000** which makes logical sense. The content in R2 (100010) is rotated to the left by 4 bits (content in R4), which means the four least significant bits (0000) will become the four most significant bit of the 32-bit number since it got rotated to the left.

[illegible]



Wave - Default

Signal	Value	Waveform
/datapath_not_tb/clk_tb	1	[Clock signal]
/datapath_not_tb/clr_tb	U	[Reset signal]
/datapath_not_tb/IncPC_tb	0	[Increment PC signal]
/datapath_not_tb/MDRRRead_tb	0	[Memory Read signal]
/datapath_not_tb/aluOp	00000	[ALU Operation signal]
/datapath_not_tb/encoderIn_tb	0000000000000000...	[Encoder Input signal]
/datapath_not_tb/RegEnable_tb	0000000000000000...	[Register Enable signal]
/datapath_not_tb/MdataIn_tb	0000000000000000...	[Memory Data In signal]
/datapath_not_tb/BusMuxOut_tb	0000000000000000...	[Bus Mux Out signal]
/datapath_not_tb/IRout_tb	UUUUUUUUUU...	[IR Out signal]
/datapath_not_tb/Zout_tb	UUUUUUUUUU...	[Z Out signal]
/datapath_not_tb/R2out_tb	UUUUUUUUUU...	[R2 Out signal]
/datapath_not_tb/R4out_tb	UUUUUUUUUU...	[R4 Out signal]
/datapath_not_tb/R5out_tb	UUUUUUUUUU...	[R5 Out signal]
/datapath_not_tb/IOut_tb	UUUUUUUUUU...	[Instruction Out signal]
/datapath_not_tb/LOut_tb	UUUUUUUUUU...	[LOut signal]
/datapath_not_tb/present_state	Reg_load1a	[Present State signal]



ones, and ones with zeros. The result will be stored in R5, and the process does not involve R4. It can be clearly seen that the right most 6 digits (100010) become 011101, which confirms the result.